

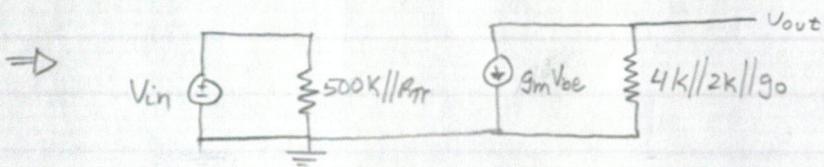


1(a) 10 points

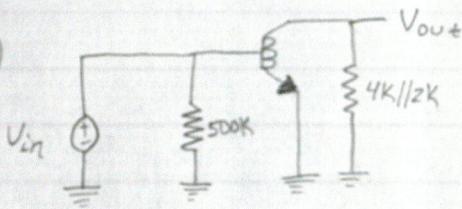

(b)

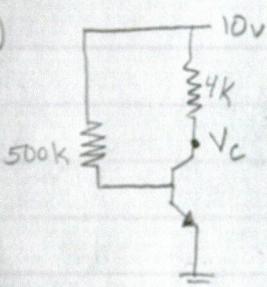

$$I_S A_E = 10^{-12} \text{ A} \quad \beta = 100$$

$$I_B = \frac{10 - (V_B - 0)}{500k} = \frac{10^{-12} \text{ A}}{100} e^{\frac{(V_B - 0)}{26mV}} \quad V_B = V_{BE} = 0.555 \text{ V}$$

$$I_C = \frac{10 - V_C}{4k} = 10^{-12} [\text{A}] \cdot e^{\frac{V_B - 0}{26mV}}$$

$$V_C = 2.444 \text{ [V]}$$

$$(c) A_V = -g_m \cdot R$$

$$g_m = \frac{I_C}{V_T}$$

$$I_C = \frac{10 - 2.444}{4k}$$

$$V_T = 26mV$$

$$g_m = 290.604$$

$$A_V = -g_m (4k // 2k)$$

$$A_V = -96.87 \left[\frac{\text{V}}{\text{V}} \right]$$

$$(d) V_{in} = 200mV \cdot \sin(\omega t + \theta)$$

$$V_{out} = A_V \cdot V_{in}$$

$$V_{out} = -19.374 \sin(\omega t + \theta) \text{ [V]}$$

$$V_{GS} - V_{DS}$$

$$(0+2) - (V_D + 2) < V_T$$

$$V_D > V_T$$

2 (a) for saturation $V_{GD} < V_T$ $V_{GS} \geq V_T$

10 points $V_T = 0.5$ $V_{IN} = 0$ $V_{GS} = 2$ $(2 - V_{DS}) < (V_T = 0.5)$

$$V_{DS} > 1.5 \quad V_S = -2$$

$$\text{so } V_D \geq -0.5 \text{ V}$$

$$\text{or } V_D > -V_T$$

$$I_{Dmin} = \frac{4 + 0.5}{R_s} = 100 \frac{\mu A}{V^2} \cdot \left(\frac{12\mu}{2\mu}\right) \cdot \left(\frac{1}{2}\right) (2 - 0.5)^2$$

$$R_s = 6.67 k\Omega$$

$$(b) R_{lmax} = 6.67 k\Omega$$

$$\text{then } R_l = \frac{1}{3} R_{lmax} = 2.22 k\Omega$$

$$\text{saturation? } I_D = \frac{4 - V_D}{2.22 k} = 100 \frac{\mu A}{V^2} \cdot \left(\frac{12}{2}\right) \left(\frac{1}{2}\right) (2 - 0.5)^2 \quad V_D = 2.5 \text{ V} \quad V_D > -V_T \quad \checkmark$$

we have saturation

$$A_V = -g_m R_{out} = -\left(100 \frac{\mu A}{V^2} \cdot \left(\frac{12}{2}\right) \cdot (2 - 0.5)\right) \cdot 2.22 k$$

$$A_V = -2 \left[\frac{V}{V}\right]$$


$$(c) V_D = V_{outT} = 2.5 \text{ V} \quad \leftarrow \text{part b}$$

$$V_{in} = 0.001 \sin(5000t + 75^\circ)$$

$$V_{out} = 2.5 - 0.002 \sin(5000t + 75^\circ)$$

[3]

10 points

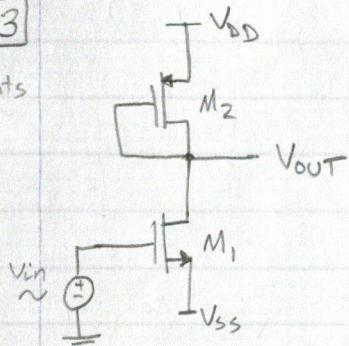


$$V_{in} = V_m \cos(\omega t + \theta)$$

$M_2 \Rightarrow$ saturation

$M_1 \Rightarrow$ saturation (given)

$$\text{then } I_{D_1} = I_{D_2}$$
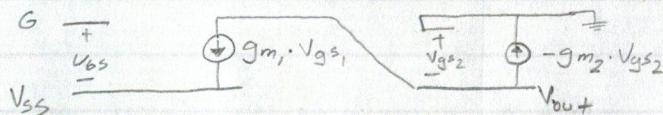
$$A_v = \frac{-V_{out}}{V_{in}} = -\frac{g_{m1}}{g_{m2}}$$



$$g_{m1} \cdot V_{in} = -g_{m2} \cdot V_{out}$$

$$V_{out} = -\frac{g_{m1}}{g_{m2}} \cdot V_m \cos(\omega t + \theta)$$

[4]

$$V_{DD} = 5V \quad V_{SS} = -2V$$

$$\frac{W_1}{L_1} = \frac{15\mu}{2\mu}$$

$$\frac{W_2}{L_2} = \frac{4.5\mu}{1\mu}$$

$$\mu_n C_{ox} = 100 \mu A/V^2$$

$$\mu_p C_{ox} = 30 \mu A/V^2$$

$$V_{Tn} = 0.5$$

$$V_{Tp} = -0.5$$

5 points

$$V_{out} \Rightarrow I_{D_1} = I_{D_2}$$

$$100 \frac{\mu A}{V^2} \cdot \frac{15}{2} \left(\frac{1}{2} \right) ((0+2) - 0.5)^2 = 30 \frac{\mu A}{V^2} \cdot \frac{4.5}{1} \left(\frac{1}{2} \right) ((V_{out}-5) + 0.5)^2$$

$$V_{out} = 0.9645 [V]$$

$$g_m = \mu C_{ox} \cdot \frac{W}{L} \cdot (V_{gs} - V_t)$$

$$g_{m1} = 100 \frac{\mu A}{V^2} \left(\frac{15}{2} \right) (0+2) - 0.5 \quad g_{m1} = 0.001125$$

$$\frac{g_{m1}}{g_{m2}} = 2.357$$

$$g_{m2} = -30 \frac{\mu A}{V^2} \left(\frac{4.5}{1} \right) ((0.9645 - 5) + 0.5) \quad g_{m2} = 0.0004773$$


$$V_{out} = -2.357 \cdot V_m \cdot \cos(\omega t + \theta)$$

$$V_{out} = 0.9645 - 2.357 \cdot V_m \cdot \cos(\omega t + \theta)$$


5

5 points

AC

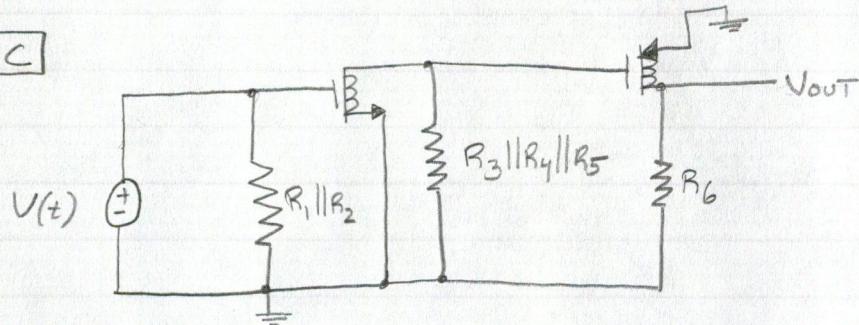


DC

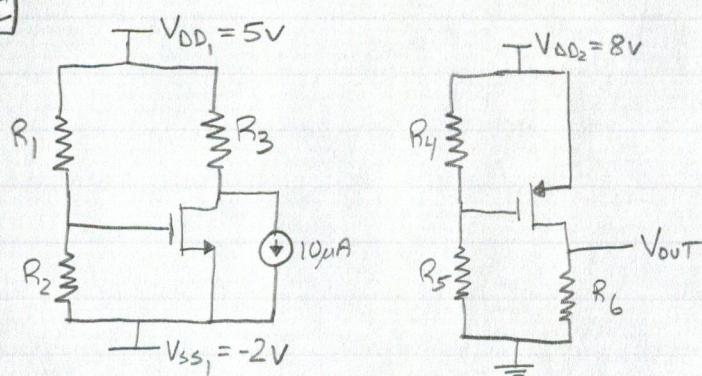


6 e) AC

10 points

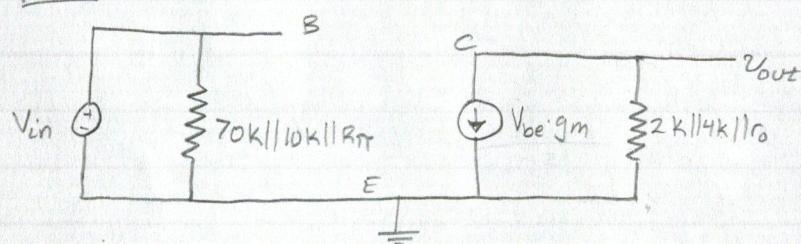

f)

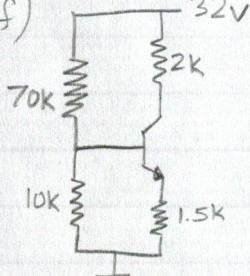

$$\frac{32 - V_B}{70K} = I_B + \frac{V_B}{10K}$$

$$I_B = \frac{J_S A_E}{B} e^{\frac{V_{BE}}{26mV}} = \frac{10^{-12}}{100} e^{\frac{V_{BE}}{26mV}}$$

$$(eq 1) \quad \frac{32 - V_B}{70K} = \frac{10^{-12}}{100} e^{\frac{V_{BE}}{26mV}} + \frac{V_B}{10K}$$

$$I_E = \frac{V_E}{1.5K} = I_B + I_C$$

$$I_B = \frac{I_E}{100}$$

$$I_E = \frac{101}{100} (I_C) \quad \text{and} \quad V_E = V_B - V_{BE}$$

$$(eq 2) \quad \frac{V_B - V_{BE}}{1.5K} = \frac{101}{100} (10^{-12}) e^{\frac{V_{BE}}{26mV}}$$

$$V_{BE} = 0.5587 \text{ V}$$

$$V_B = 3.8121 \text{ V}$$

$$I_C = \frac{32 - V_C}{2K} = 10^{-12} \cdot e^{\frac{0.5587}{26mV}}$$

$$V_C = 27.705 [\text{V}]$$

$$V_{OUT} = 0 [\text{V}]$$

g) $V_{out} = (V_{be} \cdot g_m)(2k/14k)$ $V_{be} = V_{in}$

$$A_V = \frac{V_{out}}{V_{in}} = -g_m \cdot (2k/14k) \quad g_m = \frac{L}{V_t} \quad b = \frac{32 - V_C}{2k} \quad V_t = 26mV$$

$$g_m = 0.082595$$

$$A_V = -110.127 \frac{V}{V}$$

h) $V_m = 200mV$


$$V_{in} = 0.2 \sin(\omega t + \theta)$$

$$V_{out} = A_V \cdot V_{in}$$

$$V_{out} = -22.025 \sin(\omega t + \theta)$$

7

10 points

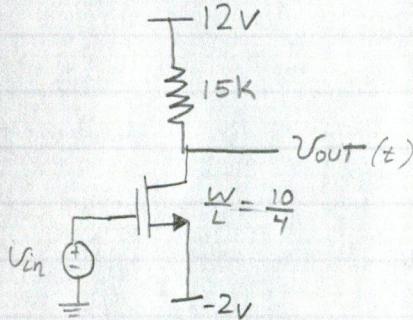

for DC $V_{gs} > V_T \quad (0+2) > 1 \quad \checkmark$

$V_{gd} < V_T \quad \leftarrow \text{check}$

$$I_D = \frac{12 - V_{out}}{15k} = 100\mu A \cdot \frac{10}{7} \left(\frac{1}{2} \right) (2 - 1)^2$$

$$V_{out} = V_D = 10.125 V$$

so $(V_{gd} = (0 - 10.125)) < (V_T = 1) \quad \checkmark \quad \underline{\text{saturation}}$

$$I_D = \frac{12 - 10.125}{15k} \quad I_D = 125\mu A$$

$$A_V = -g_m R_{out}$$


$$A_V = \frac{2 \cdot 100 \cdot R}{V_{ss} + V_T} = \frac{2 \cdot 125\mu A \cdot 15k}{-2 + 1}$$

$$A_V = -3.75 \frac{V}{V}$$


$$V_D = 10.125 V$$

8

10 points

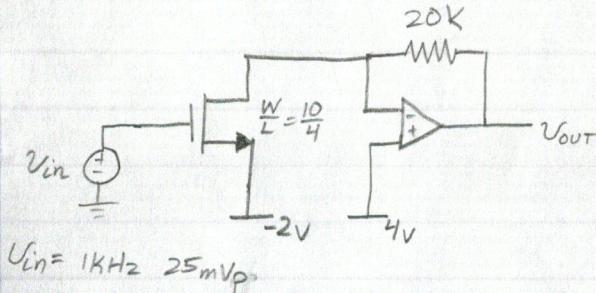

AC

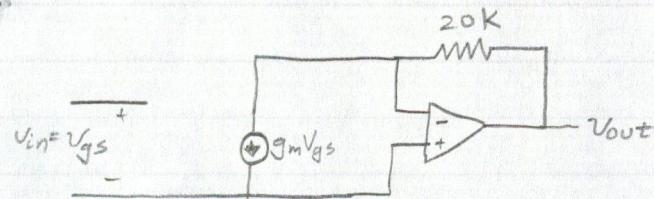

$$\frac{V_{out} - 0}{20K} = -g_m \cdot V_{gs} \quad V_{gs} = V_{in}$$

$$\frac{V_{out}}{V_{in}} = g_m \cdot 20K \quad g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{Tn})$$

$$= 100 \frac{\mu A}{V^2} \cdot \left(\frac{10}{4}\right) ((0+2)-1)$$

$$g_m = 2.5 \times 10^{-4}$$

$$V_{out} = 20K \cdot (2.5 \cdot 10^{-4}) \cdot (0.025 \sin(1000(2\pi)t))$$

$$V_{out} = 0.125 \sin(2000\pi t) \text{ [V]}$$

9

5 points



\leftarrow saturation small signal impedance is equal to V_{gm}

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GSQ} - V_T) \\ = 12 \mu A \cdot \frac{W}{L} \cdot V_{IDQ}$$

$$\frac{1}{g_m} = \frac{1}{12 \mu A \cdot \frac{W}{L} \cdot V_{IDQ}}$$




$$g_m = \frac{I_{CQ}}{V_t}$$

$$\frac{1}{g_m} = \frac{26\text{mV}}{1\text{mA}} = 26\Omega$$

10

15 points

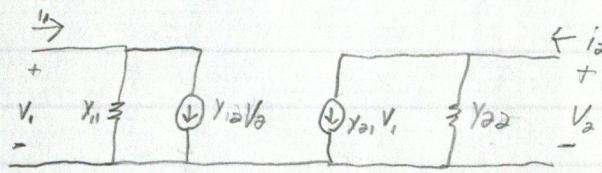

$$a) \quad y_{11} = \frac{dI_1}{dV_1} \Big|_Q \quad y_{12} = \frac{dI_1}{dV_2} \Big|_Q \quad y_{21} = \frac{dI_2}{dV_1} \Big|_Q \quad y_{22} = \frac{dI_2}{dV_2} \Big|_Q$$

$$I_1 = V_1^2 V_2^2 \quad I_2 = 0.1 e^{0.2V_1 V_2}$$

$$y_{11} = 2V_1 V_2^2 \quad y_{12} = 2V_1^2 V_2 \quad y_{21} = 0.02V_2 e^{0.2V_1 V_2} \quad y_{22} = 0.02V_1 e^{0.2V_1 V_2}$$

$$b) \quad V_{1Q} = 5V \quad V_{2Q} = 1V$$

$$y_{11} = 10 \quad y_{12} = 50 \quad y_{21} = 0.0544 \quad y_{22} = 0.2718$$


$$c) \quad I_{1Q} = V_{1Q}^2 V_{2Q}^2 = 25A \quad I_{2Q} = 0.1 e^{0.2V_{1Q} V_{2Q}} = 271.8mA$$

$$d) \quad i_1 = y_{11}V_1 + y_{12}V_2 = 110mA_{rms}$$

$$i_2 = y_{22}V_2 + y_{21}V_1 = 0.598mA_{rms}$$

11

10 points

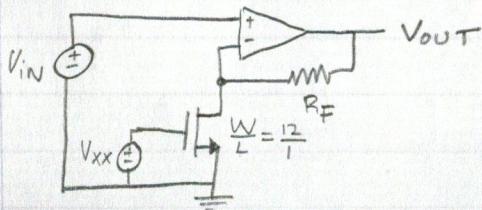

(a)

$$R_{FET} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{gs} - V_T)} \quad R_{FET} = \frac{1}{100 \frac{\mu A}{V^2} \left(\frac{12}{1}\right) (2-1)} \quad R_{FET} = 833.33 \Omega$$

$$A_V \text{ for non-inverting amplifier} = 1 + \frac{R_F}{R_{FET}}$$

$$A_V = 1 + \frac{R_F}{833.33} \left[\frac{V}{V} \right]$$

(b) $1.5 < V_{xx} < 4$

$$R_{FET} (V_{xx}=1.5) = \frac{1}{100 \frac{\mu A}{V^2} \left(\frac{12}{1}\right) (1.5-1)} \quad R_{FET} = 1666.667 \Omega$$

$$A_V (V_{xx}=1.5) = 1 + \frac{R_F}{1666.67}$$

$$R_{FET} (V_{xx}=4) = \frac{1}{100 \frac{\mu A}{V^2} \left(\frac{12}{1}\right) (4-1)} \quad R_{FET} = 277.77 \Omega$$

$$A_V (V_{xx}=4) = 1 + \frac{R_F}{277.77}$$

if R_F is large then $\frac{A_V (V_{xx}=1.5V)}{A_V (V_{xx}=4V)} \approx \frac{1}{6}$

as V_{xx} increases, the gain increases as well.

10 pts

$$12a) RFET = \frac{1}{\frac{w}{L} \mu C_{ox} (V_{xx} - V_T)} = 3,33 \text{ k}\Omega = \frac{3,33 \text{ k}}{(V_{xx} - 5)}$$

$$I = \frac{V_{in}}{RFET} \quad V_{out} = V_{in} + I \left(\frac{1}{40k} + 1E-6 \cdot s \right)^{-1}$$

$$V_{out} = V_{in} \left(1 + \frac{1}{RFET} \left(\frac{1}{40k} + 1E-6 \cdot s \right)^{-1} \right)$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{1}{RFET \left(\frac{1}{40k} + 1E-6 \cdot s \right)}$$

$$\frac{V_{out}}{V_{in}} = \frac{RFET/40k + 1E-6 \cdot RFET \cdot s + 1}{RFET/40k + 1E-6 \cdot RFET \cdot s}$$



b) see attached graphs

$$c) -\frac{1}{1E-6 \cdot 40k} = \text{poles} = -250$$


$$\text{zeros} = -1/E-6 \left(\frac{1}{40k} + 1 \right) / RFET$$

see attached plot

12)

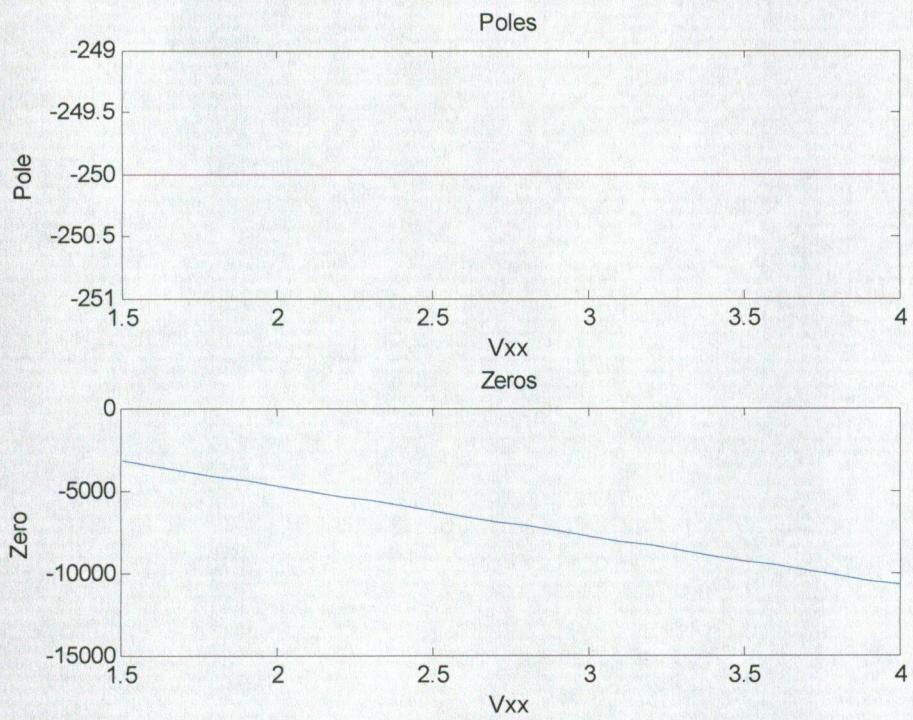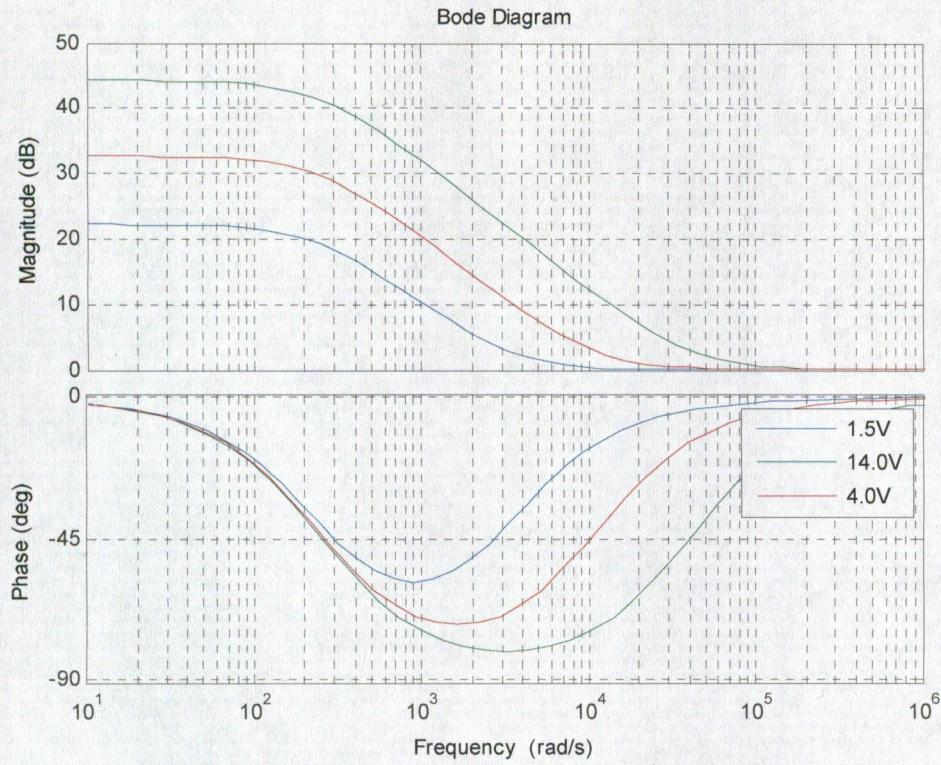

13a)

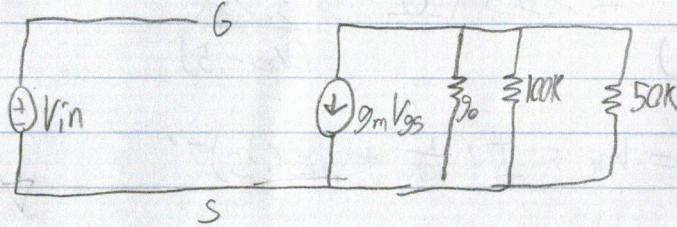

$$b) I_D = 100 \cdot 10^{-6} \cdot \frac{8}{20} (2-1)^2 = 4 \cdot 10^{-5} A$$

$$V_D = 5 - 4 \cdot 10^{-5} \cdot 100k = 1 V$$

Saturation
 $V_{DS} \geq V_T$ $V_{DS} \geq V_{GS} - V_T$

$$V_{out} = 0 V$$

$$c) g_o = \lambda \cdot I_{DQ} \quad \lambda = 1/100 \quad g_o = 4 \cdot 10^{-7} \quad R_o = 2.5 \cdot 10^6$$

$$g_m = \frac{2 I_{DQ}}{V_{GSQ} - V_T} = 8 \cdot 10^{-5}$$


$$A_v = \frac{-g_m (1/g_o + 1/R_o + 1/R_s)^{-1}}{= -2.6}$$

$$d) -20mV \cdot -2.6 = -52mV$$


$$V_{out} = -52mV \cdot \sin(\omega t + \theta)$$

[14] (a)

10 points

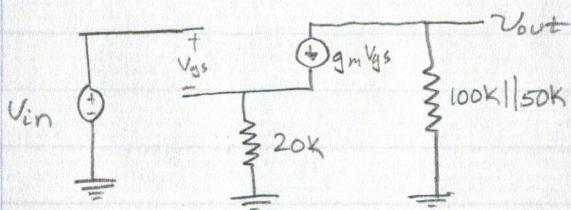

(b)

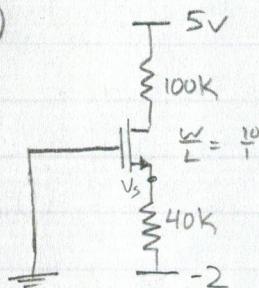

Guess Saturation

$$I_D = \frac{100\mu A}{\sqrt{2}} \left(\frac{10}{1}\right) \left(\frac{1}{2}\right) \left((0 - V_S) - 1\right)^2$$

$$I_D = \frac{V_S + 2}{40k}$$

$$V_S = -1.2 \text{ V}$$

$$I_D = 20\mu A$$

$$V_{gd} < V_T$$

$$V_d = 5 - 100k \cdot 20\mu A$$

$$V_d = 3 \text{ V}$$

$$V_{gs} > V_T$$

$$V_S = -2 + 40k \cdot 20\mu A$$

$$V_S = -1.2 \text{ V}$$

$$V_{gd} = -3 < V_T \quad \checkmark$$

$$V_{gs} = 1.2 > V_T \quad \checkmark$$

saturation

$$V_D = 3 \text{ V}$$

$$V_{out} = 0 \text{ V}$$

(c) $V_{out} = -g_m V_{gs} (100k || 50k)$

$$V_{gs} = V_{in} - (g_m V_{gs} \cdot 20k) \quad V_{gs} = \frac{V_{in}}{1 + g_m 20k}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_m}{1 + g_m 20k} (100k || 50k)$$

$$g_m = \mu_{max} \frac{W}{L} (V_{gs} - V_t) \\ = 100\mu A \cdot \left(\frac{10}{1}\right) \cdot (1.2 - 1)$$

$$g_m = 2 \times 10^{-4}$$

$$A_v = -1.333 \frac{\text{V}}{\text{V}}$$


(d) $V_m = 200 \text{ mV}$

$$V_{out} = A_v \cdot V_{in} \quad V_{in} = V_m \cdot \sin(\omega t + \theta)$$

$$V_{out} = -0.2667 \sin(\omega t + \theta)$$

15

10 points

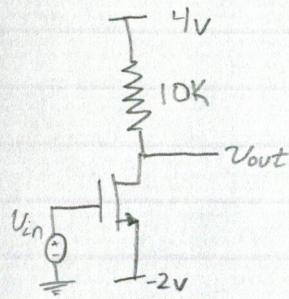

$$A_V = -8$$

$$A_V = \frac{2 \cdot I_{DQ} \cdot R_{out}}{V_{SS} + V_T}$$

$$A_V = -8 = \frac{2 \cdot I_{DQ} \cdot 10K}{-2 + 1}$$

$$I_{DQ} = 0.4 \text{ mA}$$

$$0.4 \text{ mA} = 100 \frac{\mu A}{V^2} \cdot \left(\frac{W}{L}\right)\left(\frac{1}{2}\right) \left(V_{gs} - 1\right)^2 \quad V_{gs} = (0+2)$$

$$\frac{W}{L} = 8$$

$$\text{let } W = 8 \mu \text{m} \\ L = 1 \mu \text{m}$$

check



saturation

$$V_D = 4 - 10K \cdot 10 \Omega \quad V_D = 0V$$

$$V_{gds} = (0-0) < 1$$

$$V_{gs} = 0+2 \geq 1 \quad \checkmark \text{ saturation}$$

16

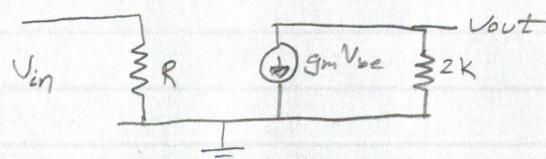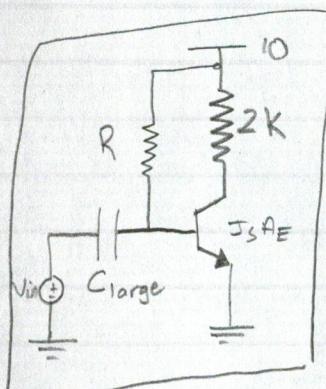

$$A_V = -8 = \frac{V_{out}}{V_{in}}$$

$$V_{out} = -2K \cdot g_m \cdot V_{be}$$

$$V_{be} = V_{in}$$

$$g_m = \frac{I_C}{V_T}$$

$$\frac{V_{out}}{V_{in}} = -8 = \frac{-2K \cdot I_C}{2.6mV}$$

$$I_C = 0.104 \text{ mA}$$

$$I_B = J_{SAE} e^{\frac{V_{be}}{V_T}}$$

$$I_B = \frac{I_C}{100} = \frac{10 - V_{be}}{R}$$

$$\text{let } V_{be} = 0.6$$

$$\text{then } R = 9M\Omega$$

$$J_{SAE} = 9.882 \times 10^{-15}$$

Verilog Code – 7 points

```

1  module Serial_2_Parallel(D_in, D_out, CLK, RST_n, EN_n);
2    input CLK;
3    input D_in;
4    input RST_n;
5    input EN_n;
6    output reg [7:0] D_out;
7
8    always @ (posedge(CLK))
9    begin
10      case(RST_n)
11        0: begin //reset data (active low)
12          D_out <= 8'b00000000;
13        end
14        1: begin //do nothing
15        end
16      endcase
17      case(EN_n)
18        0: begin //enable (active low)
19          D_out = (D_out << 1) | D_in;
20        end
21        1: begin //do nothing
22        end
23      endcase
24    end
25  endmodule

```

Verilog Test Bench simulation code – 6 points

```

1  `timescale 1ns/1ps
2
3  module Serial_2_Parallel_tb();
4    reg D_in_t;
5    reg CLK_t;
6    reg EN_n_t;
7    reg RST_n_t;
8    wire [7:0] D_out_t;
9
10   Serial_2_Parallel test(D_in_t, D_out_t, CLK_t, RST_n_t, EN_n_t);
11
12   always #10 CLK_t <= ~CLK_t;
13   initial begin
14
15     D_in_t = 0; CLK_t = 0; EN_n_t = 1; RST_n_t = 1; // start in complete disabled state
16     #20 RST_n_t = 0;
17     #20 RST_n_t = 1; //data has been reset
18     #20 EN_n_t = 0; //device enabled
19     #20 D_in_t = 1; //Data
20     #20 D_in_t = 0;
21     #20 D_in_t = 0;
22     #20 D_in_t = 0;
23     #20 D_in_t = 1;
24     #20 D_in_t = 1;
25     #20 D_in_t = 0;
26     #20 D_in_t = 1; //8 bits sent
27     #20 D_in_t = 0; //send 2 more to show operation
28     #20 D_in_t = 1;
29     #20 EN_n_t = 1; //disable
30     #20 D_in_t = 1; //shouldn't appear in D_out
31     #20 EN_n_t = 0; //reenable
32     #20 RST_n_t = 0; //show RST works
33     #20 RST_n_t = 1;
34   end
35 endmodule

```


EE 330 - F12

HW 9 – Solution

Problem 17 – Extra Credit

+ 20 Points

Test Bench Waveform – 7 points

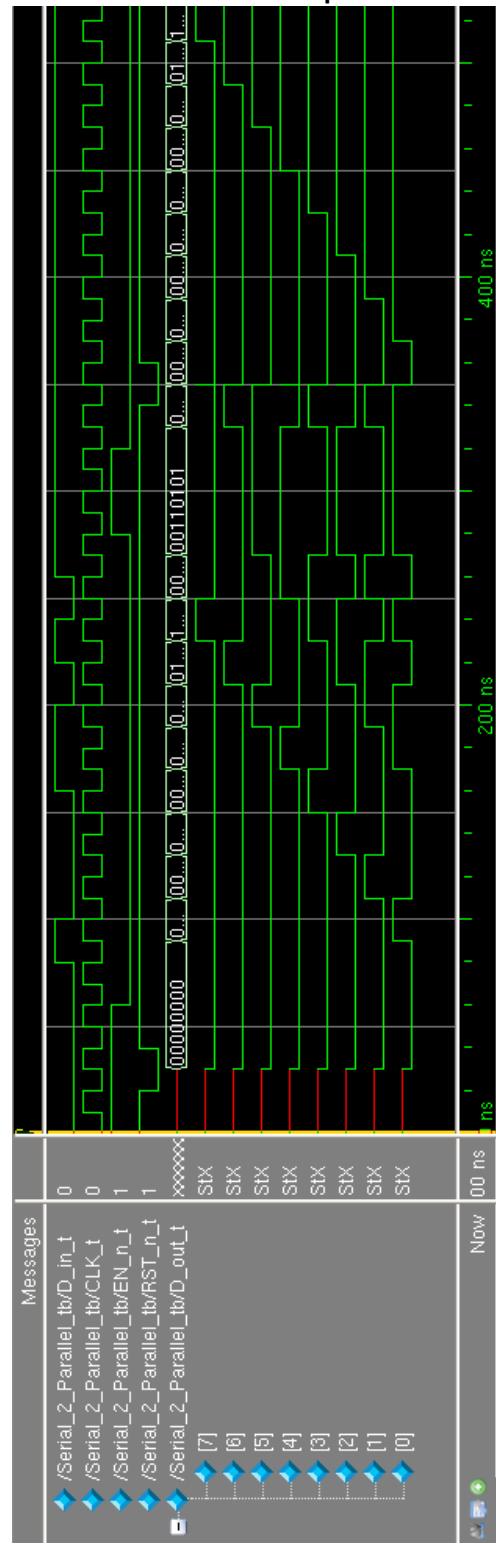

NOTE: operation of data shifting, reset and enable location