

10 pts 1.  $R = 8K$  Poly 1  $R_{\square} = 23.5 \text{ m}^2/\mu\text{m}$

Minimum Poly Width: .6  $\mu\text{m}$  Minimum Poly Spacing: .6  $\mu\text{m}$

Choose a serpentine with 14 rows

$$R = 8K = 17.2 \cdot 2 + 23.5 \cdot 14 \cdot x + (23.5 + .55 \cdot 23.5 \cdot 2) / 13$$

Contacts      rows      corners

where  $x = \# \text{ of squares per row}$

$$x = 22.26$$

Length = .6 + .6 \cdot 22.26 + .6 = 14.556  $\mu\text{m}$  > within ratio

Height = 14 \cdot .6 + 13 \cdot .6 = 16.2  $\mu\text{m}$


10 pts 2.  $C = 2 \text{ pF}$  Choose Poly - Poly 2 Capacitor:  $938 \text{ aF}/\mu\text{m}^2$

$$\frac{2 \times 10^{-12}}{938 \times 10^{-18}} = A = 2132.196 \mu\text{m}^2$$

Dimensions: 46.176  $\mu\text{m} \times 46.176 \mu\text{m}$

15 pts 3. See attached excel for results.

Layering is:

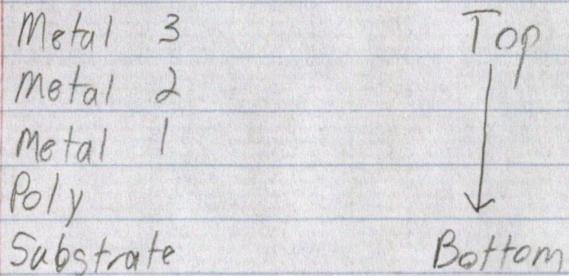

636 543 46.39

3.

Material	Material Below	Width(lambda)	Height(lambda)	Area(um^2)	C/A	Capacitance(aF)
Poly	Substrate	22	16	31.68	84	2661.12
Metal 1	Poly	6	16	8.64	56	483.84
	Substrate	6	9	4.86	27	131.22
Metal 2	Metal 1	6	8	4.32	31	133.92
	Poly	16	8	11.52	15	172.8
	Substrate	10	8	7.2	12	86.4
Metal 3	Metal 2	4	8	2.88	35	100.8
	Metal 1	6	4	2.16	13	28.08
	Poly	4	15	5.4	9	48.6
	Substrate	4	7	2.52	7	17.64

[4]

$$I = J_s \cdot A \left( e^{\frac{V_d}{V_t}} - 1 \right)$$

10 points

$$V_{d_1} = 0.55 \text{ V}$$

$$A = 50 \mu\text{m}^2$$

$$J_s = 10^{-15} \frac{\text{A}}{\mu\text{m}^2}$$

$$V_t = \frac{kT}{q}$$

assume room temp. 20°C

$$V_t = \frac{1.38065 \times 10^{23} [\text{J/K}] \cdot (273.15 + 20) [\text{K}]}{1.60217 \times 10^{19} [\text{C}]} = 0.02526 [\text{V}]$$

$$V_{d_2} = 0.65 \text{ V}$$

$$A = 50 \mu\text{m}^2$$

$$J_s = 10^{-15} \frac{\text{A}}{\mu\text{m}^2}$$

$$I_1 = (10^{-15}) (50) \left( e^{\frac{0.55}{0.02526}} - 1 \right)$$


$$I_2 = (10^{-15}) (50) \left( e^{\frac{0.65}{0.02526}} - 1 \right)$$

$$\boxed{I_1 = 1.42714 \times 10^{-4} [\text{A}]}$$

$$\boxed{I_2 = 7.4756 \times 10^{-3} [\text{A}]}$$

[5]

10 points

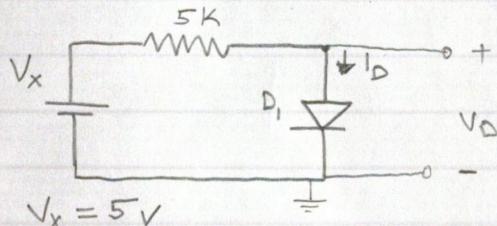

$$V_x = 5 \text{ V}$$

Guess D<sub>1</sub> is **ON**

$$I_{D_1} = \frac{V_x - V_D}{5K} = J_s \cdot A \cdot \left( e^{\frac{V_D}{V_t}} - 1 \right)$$

assume  $J_s = 10^{-15} \frac{\text{A}}{\mu\text{m}^2}$  } from previous problem  
 $A = 50 \mu\text{m}^2$   
 $V_t = 0.02526$  } #4

$$\frac{5 - V_D}{5K} = (10^{-15}) (50) \left( e^{\frac{V_D}{0.02526}} - 1 \right)$$

$$\boxed{V_D = 0.5959 [\text{V}]}$$

then

$$I_{D_1} = (10^{-15}) (50) \left( e^{\frac{0.5959}{0.02526}} - 1 \right)$$

$$\boxed{I_{D_1} = 8.808 \times 10^{-4} [\text{A}]}$$

$$V_{x_2} = 450 \text{ mV}$$

$$I_{D_2} = \frac{0.450 - V_D}{5K} = (10^{-15}) (50) \left( e^{\frac{0.450 - 0.5959}{0.02526}} - 1 \right)$$

$$V_{D_2} = 0.440607 [\text{V}]$$

$$\text{then } I_{D_2} = (10^{-15}) (50) \left( e^{\frac{0.440607}{0.02526}} - 1 \right)$$

$$\boxed{I_{D_2} = 1.8785 \times 10^{-6} [\text{A}]}$$

5 pts

6.  $R = 1,0345 \text{ K} \cdot \Omega$  @  $T = 250 \text{ K}$   $\rightarrow TCR = 100 \text{ ppm}/\text{C}$   
 $R = ?$  @  $T = 400 \text{ K}$

$$R(T_2) = R(T_1) [1 + (T_2 - T_1) TCR / 10^6]$$

$$R(400 \text{ K}) = 1,0345 \text{ K} [1 + (400 - 250) \cdot (100 / 10^6)] = 1050,02 \Omega$$

20 pts

7.

a)  $I_S = J_{Sx} A [T^m e^{-V_{SD}/kT}] = .45 \cdot 100 \cdot T^{2.3} \cdot e^{1.17/(8T/10)}$

see attached Matlab graph

b)  $I_S(27^\circ\text{C}) = 5,08 \text{ E-}13$   
 $I_S(30^\circ\text{C}) = 8,13 \text{ E-}13$

Percent Change = 60,08 % Change

see attached Matlab Code

c) Mat errors of 24,24% if it is  $2^\circ$  higher  
31,56% if it is  $2^\circ$  less

see attached Matlab Code

7.

```
clear;
clc;

%a)
Jsx = 0.45;
A = 100;
T = (0:1:100) + 273.15;
m = 2.3;
Vg0 = 1.17;
k = 1.38065E-23;
q = 1.60217E-19;
Vt = k * T / q;

Is = Jsx * A * T.^m .* exp(-Vg0 ./ Vt);

plot(T, Is);
title('Is vs T');
xlabel('Temperature(K)');
ylabel('Is(A)');


%b)
T1 = 27 + 273.15;
T2 = 30 + 273.15;
Is1 = Jsx * A * T1.^m * exp(-Vg0 / (k*T1/q));
Is2 = Jsx * A * T2.^m * exp(-Vg0 / (k*T2/q));

PercentChange = (Is2 - Is1) / Is1;

%c)
for i = 50:99
    changePositive(i) = (Is(i) - Is(i+2)) / Is(i);
end

for p = 101:-1:50
    changeNegative(p) = (Is(p) - Is(p-2)) / Is(p);
end

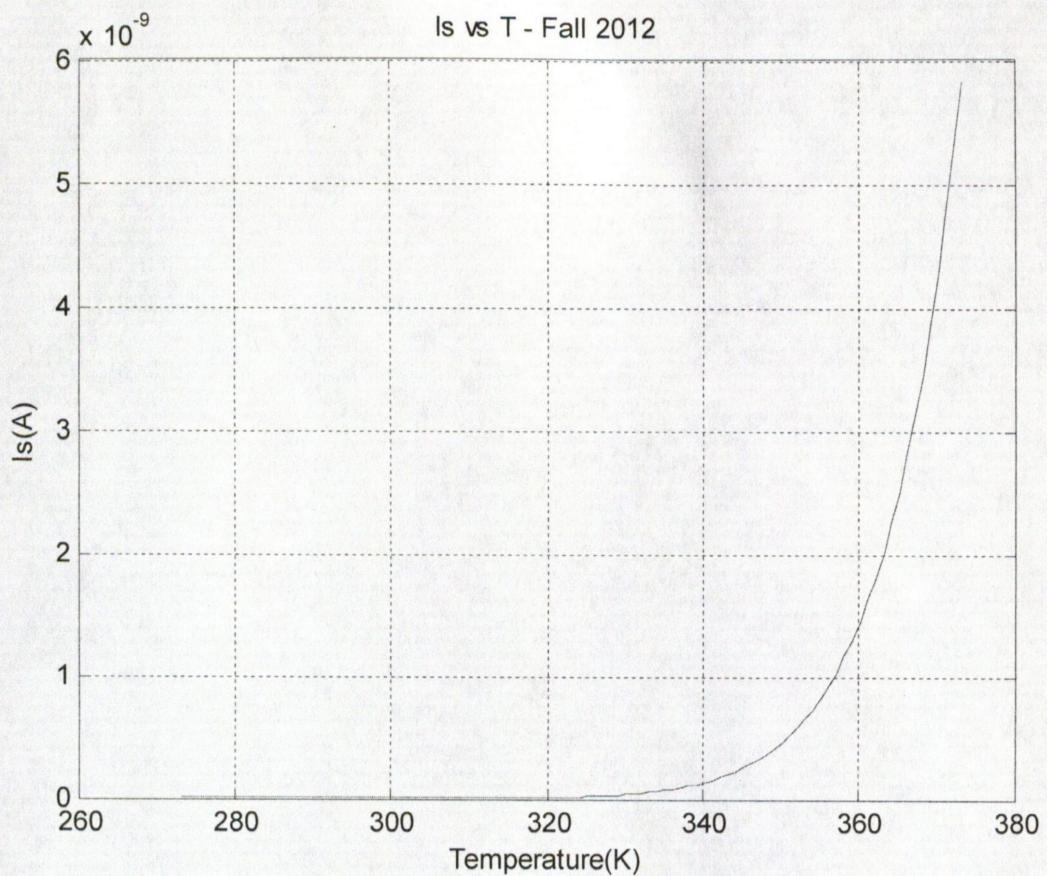maxPositive = min(changePositive);
maxNegative = max(changeNegative);
```




[8]

(2)  $HBM_1 \rightarrow V_{INT_{1-MAX}} = 250 [V]$   
 $HBM_2 \rightarrow V_{INT_{2-MAX}} = 2000 [V]$

20 points

(b)

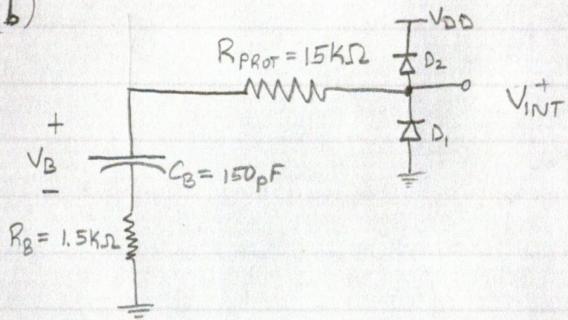


$$V_{DD} = 5 [V]$$

$$J_s = 10^{-20} \left[ \frac{A}{\mu m^2} \right]$$

$$A = 1000 [\mu m^2]$$

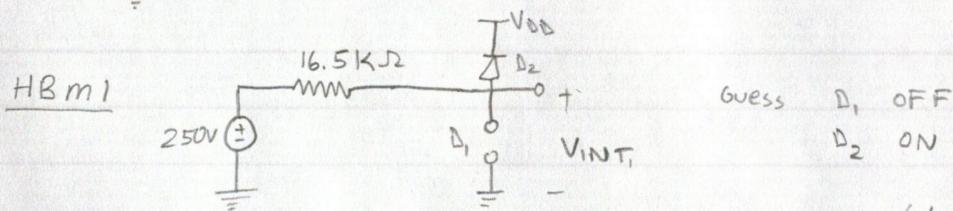
$$V_t = 0.0252617 [V] \text{ at } 20^\circ C \text{ (room temp)}$$



Guess  $D_1$  OFF       $D_2$  ON

$$I_{D2} = (10^{-20})(1000)(e^{\frac{(V_{INT_1}-5)}{V_t}} - 1) = \frac{250V - V_{INT_1}}{16.5k}$$

$$V_{INT_1} = 5.8824 [V]$$

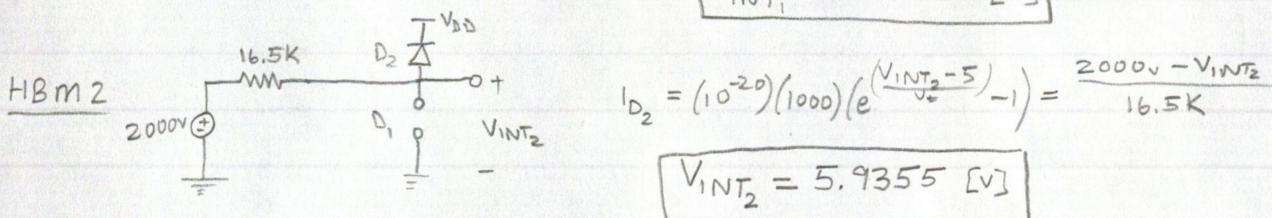

$$I_{D2} = (10^{-20})(1000)(e^{\frac{(V_{INT_2}-5)}{V_t}} - 1) = \frac{2000V - V_{INT_2}}{16.5k}$$

$$V_{INT_2} = 5.9355 [V]$$

(c) HBM1  $I_{D2_{MAX}} = (10^{-20})(1000)(e^{\frac{(V_{INT_1}-5)}{V_t}} - 1)$

$$I_{D2_{MAX}} = 14.795 [mA]$$

HBM2  $I_{D2_{MAX}} = (10^{-20})(1000)(e^{\frac{(V_{INT_2}-5)}{V_t}} - 1)$

$$I_{D2_{MAX}} = 120.85 [mA]$$


(d)  $R_{PROT}$  provides the input current something to dissipate through. Without it  $R_{IN}$  would significantly decrease, and the resultant current flow through the diodes would increase a lot, potentially damaging the protection circuit.

The Disadvantage is the added area on the die the resistor adds.

## Extra Credit

Problem 9

+10 points

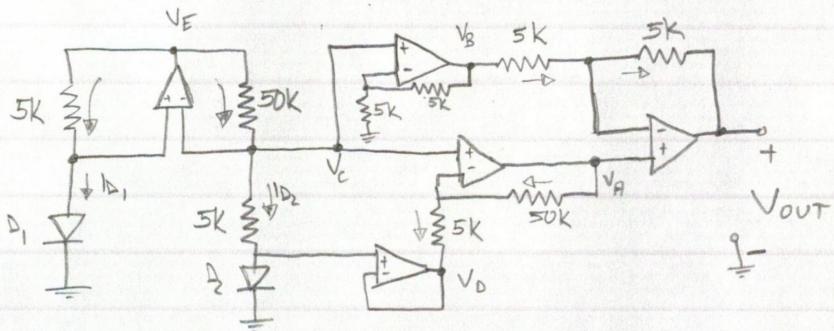

$D_1 + D_2$  matched

$$\frac{V_B - V_A}{5k} = \frac{V_A - V_{OUT}}{5k}$$

$$V_B = V_c \left(1 + \frac{5k}{5k}\right)$$

$$\frac{V_C - V_D}{5k} = \frac{V_A - V_C}{50k} \quad \text{where } V_D = V_{D_1},$$

$$I_{D_2} = (I_s) e^{\left(\frac{V_{D_2}}{V_t}\right)} - 1 = \frac{V_c - V_{D_2}}{5k}$$

$V_C = V_{D_1}$  (no current through op-amp inputs)  
 $V_{D_2} = V_D$

$$\frac{V_{D_1} - V_{D_2}}{5k} = \frac{V_A - V_{D_1}}{50k} \quad V_A = \frac{V_B + V_{OUT}}{2} \quad V_B = V_{D_1} (2)$$

$$\frac{V_{D_1} - V_{D_2}}{5k} = \frac{V_{D_1} + \frac{1}{2}V_{OUT} - V_{D_1}}{50k} \quad V_A = \frac{2V_{D_1} + V_{OUT}}{2} = V_{D_1} + V_{OUT}(\frac{1}{2})$$

$$10(V_A) - 10(V_{D_2}) = \frac{1}{2}V_{OUT} \quad V_{OUT} = 20(V_{D_1} - V_{D_2})$$

$$I_{D_1} = I_s \left( e^{\frac{V_{D_1}}{V_t}} - 1 \right) \approx I_s e^{\frac{V_{D_1}}{V_t}}$$

$$I_{D_2} = I_s \left( e^{\frac{V_{D_2}}{V_t}} - 1 \right) \approx I_s e^{\frac{V_{D_2}}{V_t}}$$

$$\frac{I_{D_1}}{I_{D_2}} = e^{\left(\frac{V_{D_1}}{V_t} - \frac{V_{D_2}}{V_t}\right)} \quad V_{D_1} - V_{D_2} = V_t \cdot \ln\left(\frac{I_{D_1}}{I_{D_2}}\right)$$

$$V_t = \frac{kT}{q}$$

$$\frac{I_{D_1}}{I_{D_2}} = \frac{\left(\frac{V_E - V_{D_1}}{5k}\right)}{\left(\frac{V_E - V_{D_2}}{50k}\right)} = 10$$

$$V_{D_1} - V_{D_2} = \frac{kT}{q} \ln(10)$$

$$V_{OUT} = 20 \cdot \frac{kT}{q} \ln(10)$$

$$10. R_o = R(0) \left[ 1 + (VCR \times V_{cross}) / 10^6 \right]$$

$$V_{out} = -\left(\frac{R_2}{R_1}\right) \cdot V_{in} \quad V_{cross} = |V_{out}|$$

$$R_1 = 1K \quad R_2(0) = 10K \quad VCR = 400 ppm$$

a)  $V_{in} = 1 \sin(2000t)$

$$|V_{ideal}| = -1V \quad |non-ideal| = -1.0004V$$

$$V_{diff} = 4E-4 V$$

b)  $V_{in} = 1 \sin(2000t)$

$$|V_{ideal}| = -10V \quad |non-ideal| = -10.04V$$

$$V_{diff} = 0.04V$$